

# EE3301 : Introduction to VLSI Design

## Homework Assignment 3

EE19BTECH11041,  
**Srijith Reddy Pakala**  
Department of Electrical Engineering  
IIT Hyderabad

November 25, 2021

### Contents

<b>1</b>	<b>SRAM Operation</b>	<b>2</b>
1.1	Problem Statement . . . . .	2
1.2	Spice Netlist . . . . .	3
1.3	Solution . . . . .	4
<b>2</b>	<b>Impact of Sizing on Performance</b>	<b>6</b>
2.1	Problem Statement . . . . .	6
2.2	Spice Netlist . . . . .	6
2.3	Solution . . . . .	7

## 1 SRAM Operation

## 1.1 Problem Statement

Static Random Access Memory (SRAM) is an important class of memory used in computers. Static refers to the fact that data is retained through feedback till the power is supplied. SRAM is faster and more expensive than Dynamic Random Access Memory (DRAM)<sup>1</sup>, and it is used in cache and registers. A standard SRAM cell consists of two cross coupled inverters which have two stable states  $Q$  and  $\overline{Q}$  to denote 0 and 1.  $M5$  and  $M6$  are the access transistors enabled by the wordline(WL) and connected to bitline(BL) and  $\overline{BL}$ . The sizing of the transistors should be such that the state is weak enough to be overpowered during a write, and yet strong enough not be disturbed during a read. We will discuss the SRAM sizing later in the course.

- (a) Implement the SRAM cell in SPICE with the following parameters: Pull down transistors M1 and M3 are of size  $8/2\lambda$ , pull up transistors M2 and M4 are of size  $3/3\lambda$ , and access transistors M5 and M6 are of size  $4/2\lambda$  (where  $\lambda = 90$ ; nm in 180 nm technology).
- (b) Verify the read operation by initializing Q and  $\overline{Q}$  to be 0 and 1 respectively. set both bitlines (BL and  $\overline{BL}$ ) to be floating 1. Verify that when the WL is enabled BL will switch to zero.
- (c) Verify the write operation by assuming Q = 0 and  $\overline{Q}$  = 1 initially. Set BL = 1 and  $\overline{BL}$  = 0. Verify that when WL is enabled Q will be overwritten from 0 to 1.
- (d) Estimate the maximum operating speed of the SRAM?

 


Figure 1


## 1.2 Spice Netlist

```
M2 Qbar Q VDD VDD pch_tt W = 270n,L=270n
M4 Q Qbar VDD VDD pch_tt W = 270n,L=270n
M1 Qbar Q 0 0 nch_tt W = 720n,L=180n
M3 Q Qbar 0 0 nch_tt W = 720n,L=180n
V1 VDD 0 1.8
M5 Qbar WL BLbar BLbar nch_tt W = 360n,L=180n
M6 BL WL Q Q nch_tt W = 360n,L=180n
V2 WL 0 PULSE(0 1 1u 1n 1n 1u 2u)
.model NMOS NMOS
.model PMOS PMOS
.lib C:standard.mos
.include "TSMC180.lib"
.tran 2u
.ic V(q) = 0 V(qbar) = 1.8 V(bl) = 1.8 V(blbar) = 1.8
.backanno
.end
```

## 1.3 Solution

(b)


Verify READ

 

WL and BL

(c)

Verify WRITE

 

(d)

Using the time delay in write mode the maximum operating speed is 7GHz.

## 2 Impact of Sizing on Performance

### 2.1 Problem Statement

Design and implement an inverter such that  $V_M = V_{DD}/2$ .

- (a) Investigate the impact of scaling factor  $S \geq 1$  (both NMOS and PMOS sizes are increased by a factor  $S$ ) on the performance of inverter in (i) no external load, and (ii)  $C_L = 20\text{pF}$  conditions. Tabulate your results.
- (b) What is the impact of increasing  $W_p$  or  $W_n$  on  $t_{pHL}$  and  $t_{pLH}$ ? Substantiate your answer by performing simulations and tabulating results.

### 2.2 Spice Netlist


```
M1 Vout N001 0 0 nch_tt W=S*0.18u,L = 0.18u
M2 Vout N001 VDD VDD pch_tt W =S*0.97u,L=0.18u
V1 VDD 0 1.8
V2 N001 0 PULSE(0 1.8 0 1f 1f 1n 2n)
.model NMOS NMOS
.model PMOS PMOS
.lib C:standard.mos
.include "TSMC180.lib"
.tran 2n
.meas tpHL TRIG V(n001)=0.9 RISE=1 TARG V(vout)=0.9 FALL=1
.meas tpLH TRIG V(n001)=0.9 FALL=1 TARG V(vout)=0.9 RISE=1
.meas tp PARAM (tpLH+tpHL)/2
.step param S 1 10 1
.backanno
.end
```

## 2.3 Solution

$V_{DD} = 1.8V$  and  $V_M = 0.9V$ . By trial and error to get  $V_M = V_{DD}/2$  the design parameters obtained at  $S=1$  are:  $\beta = 5.39 = 0.97/0.18$ .

(a)  
(i)


No external Load

 

$V_{in}$  and  $V_{out}$  at  $S=1$

- $t_p = 6.66$  psec at  $S = 1$

S	tpLH (psec)	tpHL (psec)	tp (psec)
1	5.32	8	6.66
2	5.62	10.3	7.97
3	5.82	11.3	8.56
4	5.85	11.8	8.86
5	5.94	12.2	9.08
6	5.89	12.4	9.19
7	5.98	12.6	9.33
8	6.02	12.8	9.43
9	6.04	12.9	9.5
10	6.04	13.0	9.55

 


$t_p$  Vs S (No external Load)

- The propagation delay is almost constant in the absence of external load.



(ii)


When  $C_L = 20\text{pF}$

 

$V_{in}$  and  $V_{out}$  at  $S=1$

- $t_p = 96\text{ nsec}$  at  $S = 1$

S	tpLH (nsec)	tpHL (nsec)	tp (nsec)
1	77.1	115.2	96.2
2	40.4	73.7	57.1
3	27.3	53.4	40.4
4	20.6	41.8	31.2
5	16.5	34.3	25.4
6	13.8	29.1	21.5
7	11.9	25.3	18.6
8	10.4	22.3	16.3
9	9.29	20	14.6
10	8.38	18.1	13.2

 

$t_p$  Vs S (No external Load)

• The propagation delay decreases with scaling in presence of capacitance.


(b) If we increase  $W_p$ ,  $\beta$  increases. Therefore we seeing the impact of changing  $\beta$  here.

$W_p$	$W_n$	$t_p$ (nsec)
0.97u	0.18u	6.9
1.07u	0.18u	7.25
1.17u	0.18u	7.65
1.27u	0.18u	8.08
1.37u	0.18u	8.43
1.47u	0.18u	8.93
1.57u	0.18u	9.27
1.67u	0.18u	9.51
1.77u	0.18u	10.04
1.87u	0.18u	10.2

- As  $\beta$  increases, Propagation delay  $t_p$  increases.
 
## Sizing of Inverters

③ Given  $C_i = 10 \text{ fF}$ ,  $C_L = 20 \text{ pF}$ ,  $t_{p0} = 70 \text{ ps}$ ,



④  $\gamma \approx 1$   $F = \frac{C_L}{C_i} = 2000$ ,  $N = 3$

$$f = \sqrt[N]{F} = \sqrt[3]{2000} = 12.599$$

$$S_1 = 1, S_2 = f = 12.599, S_3 = f^2 = 158.74$$

$$t_p = t_{p0} N \left[ 1 + \frac{f}{\gamma} \right] = 70 \text{ p} \times 3 \times (13.599)$$

$$\boxed{t_p = 2.855 \text{ n}}$$

⑥ To achieve minimum delay we can change no of stages

At minimum  $t_p$ .

$$f = e^{\left(1 + \frac{\gamma}{f}\right)} = e^{\left(1 + \frac{1}{f}\right)}$$

$$f = 3.591 \approx 3.6$$

③

⑥

$$N = \frac{\ln(F)}{\ln(f)} = \frac{\ln(2000)}{\ln(3.6)} = 5.9454 \approx 6$$

If we don't need inverted output we can use  $N=6$

$$\underline{N=6}$$
$$t_p = N t_{p0} \left( 1 + \frac{f}{\gamma} \right) = 6 \times 70 \text{p} (4.6) = 1.932 \text{ns}$$

If we need to have only inverted output we can use  $N=5$

Since  $N=5$  is odd.

$$\underline{N=5}$$

$$t_p = N t_{p0} \left( 1 + \frac{f}{\gamma} \right) = 5 \times 70 (5.57) = 1.95 \text{ns}$$

$$f = \sqrt{2000} = 4.573$$

③ ⑦ In case ⑥ delay is less but requires more area compared to ⑦.

(3)

(d)

$$\text{Dynamic power} = C_{\text{Total}} V_{DD}^2 \text{freq}$$

$$\text{Here } C_{\text{Total}} = \sum C_i$$

$$= C_1 + C_2 + \dots + C_N$$

$$= (C_i + fC_i + f^2C_i + C_L)$$

$$= C_i \frac{(f^4 - 1)}{(f - 1)}$$

$$\text{freq} = \frac{1}{2 \times t_p} = \frac{1}{2 \times 2.855 \times 10^{-9}} = \cancel{175.33 \text{ MHz}} \cdot \cancel{24.39 \text{ MHz}} = 175 \text{ MHz}$$

$$P_{\text{dynamic}} = C_i V_{DD}^2 \frac{(f^4 - 1)}{(f - 1)} \times \frac{1}{2N^2 t_{p0} \left(1 + \frac{f}{f_0}\right)}$$

$$= 10 \times 10^{-15} \times (2.5)^2 \times (175.33) \times 10^6 \times \frac{((12.6)^4 - 1)}{(11.6)}$$

$$P_{\text{dynamic}} = 24.39 \text{ mW}$$

## CMOS LOGIC


④ Given  $f(A, B, C, D) = \overline{A \cdot (B \cdot (C + D) + C \cdot D)}$

$$L_{\min} = L_N = L_P = 180\text{nm}/250\text{nm}$$

$$R_P = 2R_N \text{ for same drive length.}$$

Now we will multiply  $W_P$  or  $W_N$  to make optimal wr.

## CMOS LOGIC

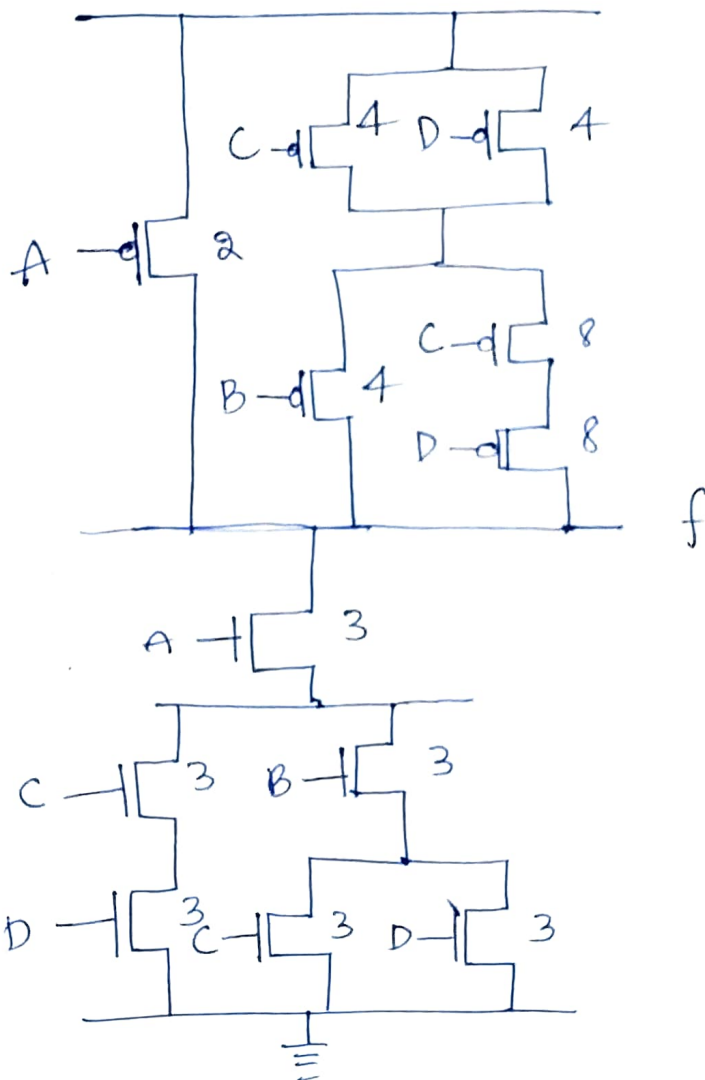

The number beside NMOS & PMOS represents width scale.

Worst case scenario :  $t_{pHL} = t_{pLH} = 0.69R_N C_L$

5

# CMOS Inverter

Given  $V_{t,n} = 0.2V$ ,  $|V_{t,p}| = 0.3V$ .

$R_n = 2K\Omega * \mu m$ ,  $R_p = 3K\Omega * \mu m$ ,  $V_{DD} = 1V$

$W_p = W_n = 1\mu m$

NMOS ON:  $R_{on,n} = \frac{R_n}{W_n} = 2K\Omega$


PMOS ON:  $R_{on,p} = \frac{R_p}{W_p} = 3K\Omega$

## Region ①

$0 < V_{in} < V_{t,n}$

PMOS  $\rightarrow$  ~~ON~~  $= ON$

 NMOS  $\rightarrow V_{gs} < V_{t,n} \rightarrow OFF$




$V_{out} = V_{DD} = 1$

## Region ② :

$V_{t,n} < V_{in} < V_{DD} - |V_{t,p}|$

PMOS  $\rightarrow ON$

NMOS  $\rightarrow ON$

 




5

Region ③

$$V_{in} > V_{DD} - |V_{tp}| = 0.7V$$


PMOS  $\rightarrow V_{sg} < |V_{tp}| \rightarrow \text{OFF}$

NMOS  $\rightarrow \text{ON}$

 

$$V_{out} = 0V$$

VTC

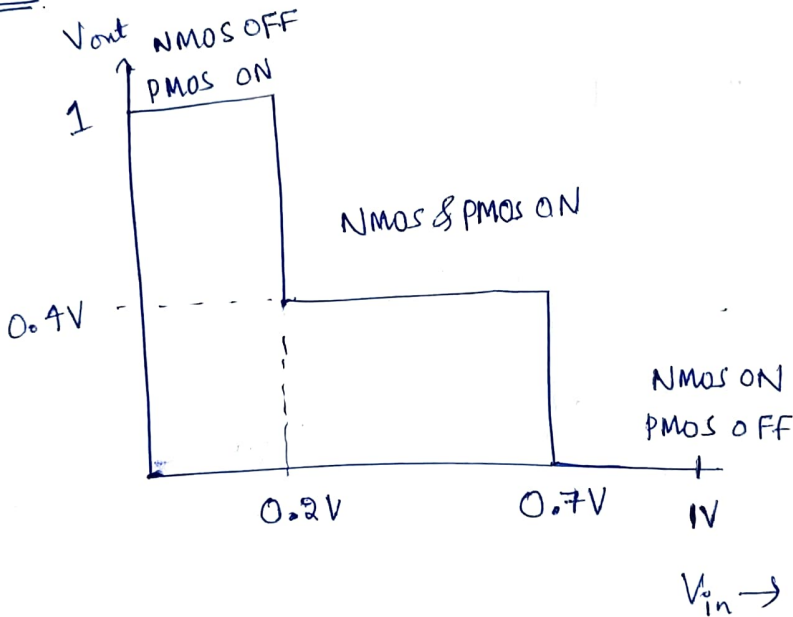

\* THE END \*